



Faculty of Engineering and Technology
Electrical and Computer Engineering Department
Advanced Digital Design ENCS3310

Homework#2

- Write a behavioral Verilog description for the state diagram shown in figure1.
- Write a Structural Verilog description for the circuit shown in figure 2 (i.e. build a D-FF then use it to build the circuit structurally).
- Write a Structural Verilog description for the circuit shown in figure 3 (hint: you can modify the code in part b above).
- Write a test bench that will take instance from the module in part a and and instance from the module in part b and print "PASS" if they have identical output and fail if they haven't .
- Write a test bench that will take instance from the module in part a and and instance from the module in part c and print "PASS" if they have identical output and fail if they haven't .

 


Figure 1

 


Figure 2

 


Figure 3